

Electronics and Communication Engineering Department

National Institute Of Technology, Trichirappalli\_620015

Time: 3 Hours

EC 306 Microwave Components and Circuits

Max.Marks:50

NB: Write down the missing word/expression/value/Fig. wherever blank is to be filled.

1. a. Effective Dielectric constant is to be taken in the case of Microstrip line because of \_\_\_\_\_.
  - b. The cross section of an ANTIPODAL FINLINE is \_\_\_\_\_.  
It is useful for \_\_\_\_\_.
  - c. NON TEM mode is supported by \_\_\_\_\_.
  - d. The scattering matrix of a matched isolator with 1 dB insertion loss and 30 dB Isolation is given by \_\_\_\_\_.
  - e. The CPW mode is otherwise called as \_\_\_\_\_ mode.
  - f. The S matrix of an ideal transmission line is \_\_\_\_\_.
  - g. In Microstrip when the EM wave propagates in y direction, the components \_\_\_\_\_ and \_\_\_\_\_ are NON ZERO.
  - i. The difference in S matrix of a power divider and that of Wilkinson is \_\_\_\_\_ . (10 Marks)
2. a. Show that there is no power coming out of the ISOLATED port of a waveguide directional coupler.
  - b. The Directivity of an Ideal directional coupler is \_\_\_\_\_.
  - c. Two identical directional couplers are placed in a waveguide to sample the incident and reflected power. The meter shows the power level of the reverse coupler to be 10 dB down from the level of the forward coupler. The VSWR in the guide is \_\_\_\_\_. (4 +2 +4) Marks
3. Specifications for a low pass microstrip filter are as given below. Design and Draw the Layout for the third order filter with cut off frequency = 1 GHz, pass band ripple = 0.1 dB, source and load I impedance = 50 ohms , effective  $\epsilon = 10.8$ ,

thickness = 1.27 mm. w/h for 20 ohms, 50 ohms and 100 ohms are 2, 1 and respectively.

$$g_0 = g_4 = 1, \quad g_1 - 1.0316 = g_3 \quad \text{and} \quad g_2 = 1.474.$$

(10) Marks

4. a. From the first principle, obtain the design parameters of series and shunt branch of a  $90^\circ$  branch line coupler

b. Hence or otherwise find the Impedance values of series and shunt arm of a stripline branch line coupler assuming the characteristic Impedance to be  $Z_0$ .

(7 + 3) Marks

5. a. The value more than \_\_\_\_\_ is said to be HIGH VSWR. In such a measurement the distance between successive minima is found to be 1.5 cm. The distance between 3 dB minima points are 0.1 cm. The corresponding VSWR is \_\_\_\_\_.

b. In the Microwave Impedance measurement for the Load VSWR is 2, the distance between successive minima was 1.5 cm. The shift in minima was 0.75 cm towards source. Use the Smith Chart and find the load impedance.

c. In a Microwave frequency measurement, the successive minima distance is found to be 2.43 cm, the wider dimension of the waveguide is 2.286 cm. The frequency of operation is \_\_\_\_\_ GHz.

(4 + 3 + 3) Marks